

Implementations of Quantum Adders and Quantum Modular Adders

Hao-Chien Wang

Department of Physics, National Taiwan University

March 26, 2020

Outline

- 1 Introduction
- 2 Draper's adder
- 3 Beauregard's modular adder
- 4 Implementation
- 5 References

Introduction

- Starting point: Paper by Archimedes Pavlidis and Dimitris Gizopoulos [1].
- Building block 1: Adder on Fourier basis by T. Draper[2].
- Building block 2: Modular adder by S. Beauregard[3].
- Building block 3: Modular multiplier by S. Beauregard[3] (will be covered by 宥韻).
- Current result: U_a using $2n + 3$ qubits

All scripts are on my Github repo:

https://github.com/fhcwcsy/qc_practice/tree/master/shor_s_algorithm

Eigenvalues and Eigenvectors of U_a

$$U|u_s\rangle = e^{\frac{2\pi is}{r}} |u_s\rangle$$
$$|u_s\rangle = \frac{1}{\sqrt{r}} \sum_{k=0}^{r-1} e^{\frac{-2\pi isk}{r}} \left| x^k \bmod N \right\rangle$$

It can be proved that

$$\frac{1}{\sqrt{r}} \sum_{t=0}^{r-1} |u_t\rangle = |1\rangle$$

Therefore, we estimate the eigenvalues to obtain $\frac{s}{r}$.

Proof: Eigenvalues and Eigenvectors

$$\begin{aligned} U|u_s\rangle &= U \frac{1}{\sqrt{r}} \sum_{k=0}^{r-1} e^{\frac{-2\pi i s k}{r}} |x^k \bmod N\rangle \\ &= \frac{1}{\sqrt{r}} \sum_{k=0}^{r-1} e^{\frac{-2\pi i s k}{r}} |x^{k+1} \bmod N\rangle \\ &= \frac{1}{\sqrt{r}} \sum_{k=0}^{r-1} e^{\frac{-2\pi i s (k-1)}{r}} |x^k \bmod N\rangle \\ &= e^{\frac{2\pi i s}{r}} |u_s\rangle \end{aligned}$$

Proof: Sum of Eigenvectors is $|1\rangle$

$$\begin{aligned}\frac{1}{\sqrt{r}} \sum_{t=0}^{r-1} |u_t\rangle &= \frac{1}{\sqrt{r}} \sum_{t=0}^{r-1} \frac{1}{\sqrt{r}} \sum_{k=0}^{r-1} e^{\frac{-2\pi i t k}{r}} |x^k \bmod N\rangle \\ &= \frac{1}{r} \sum_{k=0}^{r-1} \left(\sum_{t=0}^{r-1} e^{\frac{-2\pi i t k}{r}} \right) |x^k \bmod N\rangle \\ &= \frac{1}{r} \sum_{k=0}^{r-1} (\delta_{k,0} r) |x^k \bmod N\rangle \\ &= |1\rangle\end{aligned}$$

Review: Quantum Fourier Transform

Define:

$$e(t) \equiv e^{2\pi it}$$

$$|\phi_k(a)\rangle \equiv \frac{1}{\sqrt{2}} \left(|0\rangle + e\left(\frac{a}{2^k}\right) |1\rangle \right)$$


$$\frac{a}{2^k} = 0.a_k a_{k-1} \cdots a_2 a_1$$

$$R_k = \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & e\left(\frac{1}{2^k}\right) \end{pmatrix}$$

QFT:

$$|a\rangle \xrightarrow{F_{2^n}} \frac{1}{2^{\frac{n}{2}}} \sum_{k=0}^{2^n-1} e\left(\frac{ak}{2^n}\right) |k\rangle = |\phi_n(a)\rangle \otimes \cdots \otimes |\phi_2(a)\rangle \otimes |\phi_1(a)\rangle$$


QFT Circuit

 

$$\begin{aligned}
 |a_n\rangle &\xrightarrow{\text{Hadamard}} \frac{1}{\sqrt{2}}(|0\rangle + e(0.a_n)|1\rangle) \\
 &\xrightarrow{C_{n-1}-R_2} \frac{1}{\sqrt{2}}(|0\rangle + e(0.a_n a_{n-1})|1\rangle) \\
 &\quad \vdots \\
 &\xrightarrow{C_1-R_n} \frac{1}{\sqrt{2}}(|0\rangle + e(0.a_n a_{n-1} \cdots a_1)|1\rangle) \\
 &= |\phi_n(a)\rangle
 \end{aligned}$$

Draper's Fourier Adder


$$|\phi(a)\rangle \rightarrow |\phi(a+b)\rangle$$

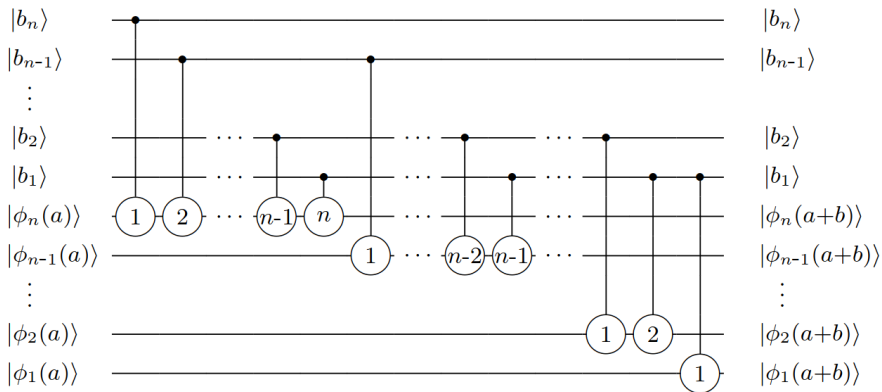

Tracing Draper's Adder

$$\begin{aligned}
 |\phi_n(a)\rangle &\xrightarrow{C_{b_n-R_1}} \frac{1}{\sqrt{2}} \left(|0\rangle + \left[e(0.a_n a_{n-1} \cdots a_1 + 0.b_n) \right] |1\rangle \right) \\
 &\xrightarrow{C_{b_{n-1}-R_2}} \frac{1}{\sqrt{2}} \left(|0\rangle + \left[e(0.a_n a_{n-1} \cdots a_1 + 0.b_n b_{n-1}) \right] |1\rangle \right) \\
 &\quad \vdots \\
 &\xrightarrow{C_{b_1-R_n}} \frac{1}{\sqrt{2}} \left(|0\rangle + \left[e(0.a_n a_{n-1} \cdots a_1 + 0.b_n b_{n-1} \cdots b_1) \right] |1\rangle \right) \\
 &= |\phi_n(a+b)\rangle
 \end{aligned}$$

Parallel Adder

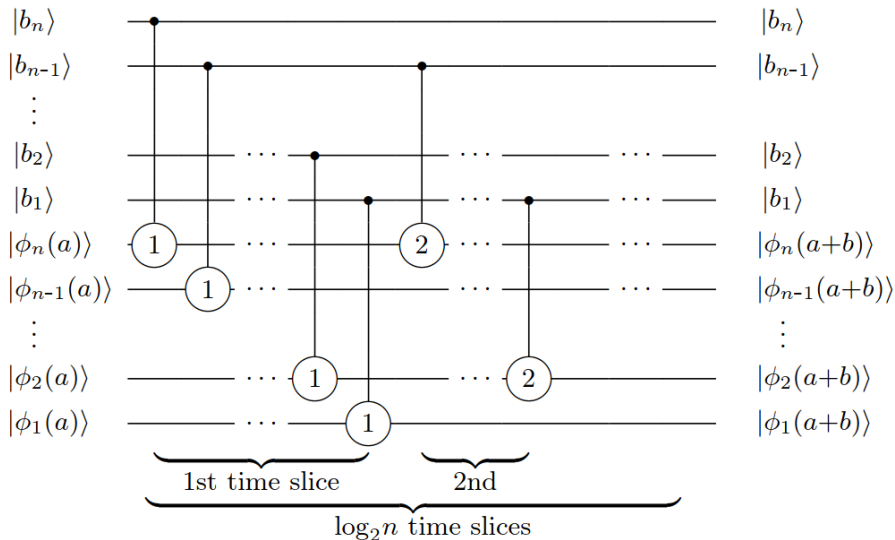


Beauregard's Modular Adder

$$\Phi ADD(a)MOD(N) |\phi(b \bmod N)\rangle = |\phi(a + b \bmod N)\rangle$$


- Qubits
 - Use 2 controls (1 for $C - U_a$, 1 for building modular multiplier).
 - 1 ancilla qubit (must be cleared).
 - Use one more qubit to store a to prevent overflow and detect sign (check MSB).
- Adding numbers larger than N can be reduced.
- Steps:
 - 1 Add a
 - 2 Subtract N
 - 3 Convert to Computational basis, check MSB. Add N back if MSB is 1.
 - 4 Clear the ancilla bit using

$$a + b \bmod N \geq a \iff a + b < N$$

Beauregard's Modular Adder

 

Final Gate (for now)

 

- Currently complete:
 - Adder
 - Modular adder
 - Modular Multiplier
- Obstacle: the circuit is too big to get the correct result using real device.

References

- [1] Pavlidis, Archimedes, and Dimitris Gizopoulos. “Fast Quantum Modular Exponentiation Architecture for Shor’s Factorization Algorithm.” *arXiv preprint* arXiv:1207.0511 (2012).
- [2] Draper, Thomas G. “Addition on a quantum computer.” *arXiv preprint* quant-ph/0008033 (2000).
- [3] Beauregard, Stephane. “Circuit for Shor’s algorithm using $2n+3$ qubits.” *arXiv preprint* quant-ph/0205095 (2002).